| Glossary of terms  |  |  |  |  |
|--|--|--|--|--|
|  |  |  |  |  |
|  |  |  |  |  |
| To enable a first time builder to understand the terms we use on a kit build, many will be first time builders |  |  |  |  |
| and as such will be ex   | periencing different methods of manufacture.                   |  |  |  |
| <u>Term</u>  | <u>Explanation</u>   |  |  |  |
|  |  |  |  |  |
| NOS  | New old stock or new materials sitting in stock for masy years |  |  |  |
|  |  |  |  |  |
| NIB  | New in box   |  |  |  |
| DOLLO  | Deduction of homeodesic substances in local force colling      |  |  |  |
| ROHS   | Reduction of hazardous substance ie lead free solder           |  |  |  |
| mu   | Valve gain valueecc88 is 33mu                                  |  |  |  |
|  |  |  |  |  |
| opamp  | A solid state amplifer used as a sub driver in a Allegro       |  |  |  |
|  |  |  |  |  |
| Point to point   | A method of wiring components using wire and turrets           |  |  |  |
| DOD  | Defends of a fine with the seconds                             |  |  |  |
| PCB  | Printed circuit boards   |  |  |  |
| RIAA   | Recording Institute of America                                 |  |  |  |
|  | The equalisation curve is the standard phono stages use        |  |  |  |
|  | Lint audio DOES NOT adhere to this standard                    |  |  |  |

| Frequency response |   |
|--------------------|---|
| THD                | Total harmonic distortion   |
| RCA plug           | A standard audio input and output plug  |
| B9a socket         | 9 pin miniature valve socket  |
| B7g socket         | 7 pin miniature valve socket  |
| Octal socket       | 8 pin valve socket and also used in industrial relays                                   |
| SMPS               | Switch mode power supply  |
| Linear regulator   | Lint uses a LM317 and LM7806 on heater supplies for accurate dc supplies and noise free |
| Twisted pair       | A pair of cables twisted to reduce rf interference.                                     |
| RF shield          | A shield preventing external radio noise entering                                       |
| Magnetic shield    | Steel being used to prvent magnetic noise ingress into audio system                     |
| Impedance          | Resistance of a circuit output speaker impedance  |
| Sensitivity        | The signal to enable system to provide a given output                                   |
| BIAS               | Determine current flowing through a valve and sets optimum operating point              |

| Shipping terms           |   |  |
|--------------------------|---|--|
| SKD                      | Semi knocked down   |  |
| CKD                      | Complete knock down   |  |
| CKB                      | Complete knock down   |  |
| CBU                      | Fully built up  |  |
| FOB                      | Free on board   |  |
| CIF                      | Cost insurance and freight                                    |  |
| Valves used (Tubes in US | 1   |  |
|                          |   |  |
| EZ80                     | Rectifier heater 6v3, B9a base max 350 volts                  | Retired and available NOS maybe used in Classic 12 and Semplice /Allegro |
| EZ81                     | Rectifier heater 6v3, B9a base max 350 volts                  | New production, maybe used in all monoblocks and pre amps                |
|                          | Higher current than EZ80 but maybe used in EZ80 circuitry     |  |
|                          |   |  |
| 6x4/EZ90                 | Rectifier heater 6v3, B7g and used with an adaptor            | Reired and desirable on pre amp especially Sylvania and all black plates |
|                          | Max 375 volts   |  |
| ECC88                    | Dual triode B9a   | Current production   |
| 6922                     | Dual triode B9a   | Current production   |
|                          |   |  |
| 6n1p                     | Dual triode b9a higher heater current than ECC88              | Retired but NOS available used in monoblocks and desirable               |
| 5670                     | Dual triode similar to Russian 6n3p B9a                       | Retired but NOS plentiful different pin out to ECC88                     |
| 6n3p                     | Dual triode B9a   | Retired but NOS plentiful and second choice on pre amps to 5670          |
| EL84                     | Power pentode   | New production   |
| 6p15p                    | Power penrtode compatible with EL84 with small change to bias | Retired but NOS plentiful and very nice in Series 12                     |
| 6p14p-ev                 | Same as EL84M high voltage 7189                               | Retired but very much desirable used in Clasisc 12                       |
|                          |   |  |
| 1n4007                   | Solid state rectifier diode 1 amp                             |  |